

# Gas Discharge Tube: Application Note




## Application

### ■ Signal & High Frequency protection

#### a. Telephone, Fax, Modem, VOIP...etc user's terminal equipments


Once the transient over-voltage occurs, the GDT will spark over to protect the vulnerable components in the communication terminal equipments by guiding the surge to the ground.

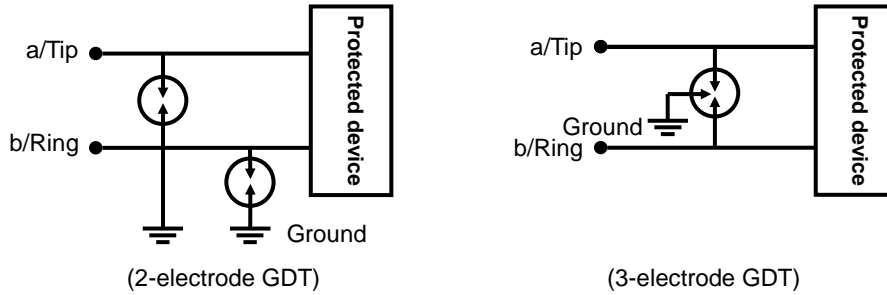

(Fig.1)

#### b. Signal Line Protection


GDT is connected in parallel between two signal lines to suppress the surge potential differences in the input.

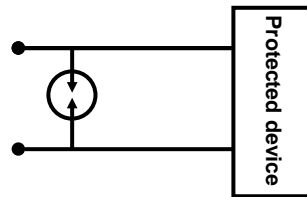

(Fig.2)

#### c. CATV/Coaxial Line/Video System Protection


Because of their very low self-capacitance, the GDTs are well-suited in the high frequencies fields, such as CATV networks, video system, coaxial line, cathode ray tube, etc.

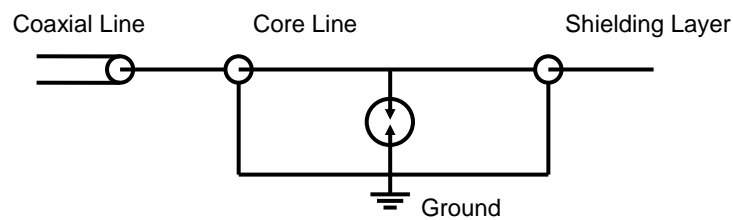

(Fig.3)

### ■ AC Line Protection

GDT combined with varistors can offer an ideal solving project to protect all kinds of installations from being damaged by transient over-voltage coupled into AC power networks.

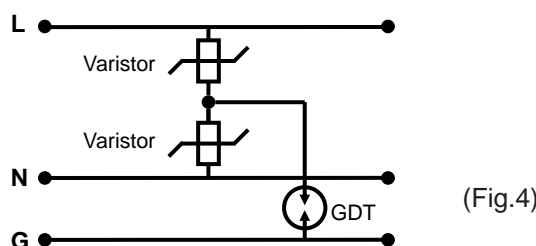

(Fig.4)